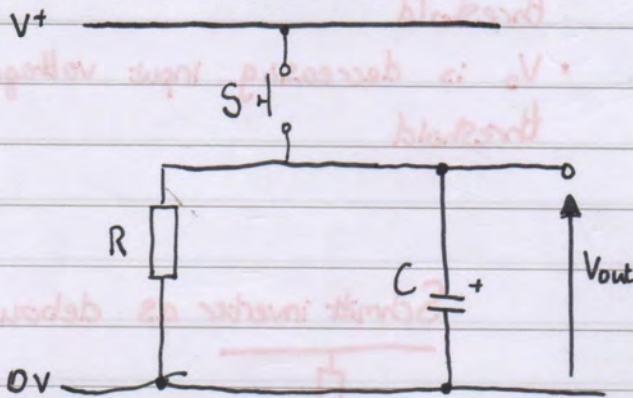



## ET2 Questions



K	$\times 10^3$	m	$\times 10^{-3}$
M	$\times 10^6$	$\mu$	$\times 10^{-6}$
G	$\times 10^9$	n	$\times 10^{-9}$

- The time constant is equal to  $RC$
- $0.69 RC$  gives  $\frac{1}{2} V^+$

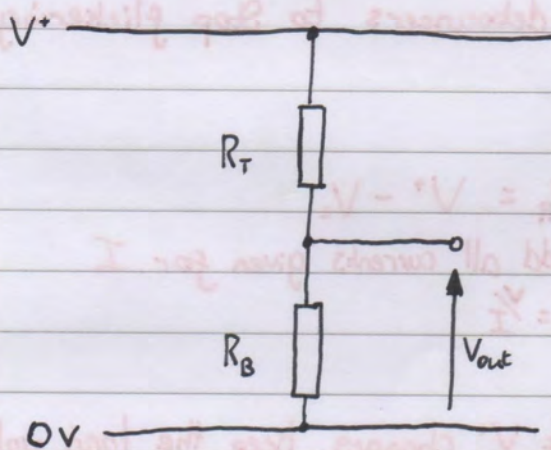- If charging,  $0.63 V^+$  gives  $RC$
- If discharging,  $0.37 V^+$  gives  $RC$
- $V^+$  reaches  $0V$  at approximately  $5RC$




$$I = \frac{V^+}{R_T + R_B}$$


$$V_{oc} = I \times R_B$$

$$I_{sc} = \frac{V^+}{R_T}$$

$$R_o = \frac{V_{oc}}{I_{sc}}$$

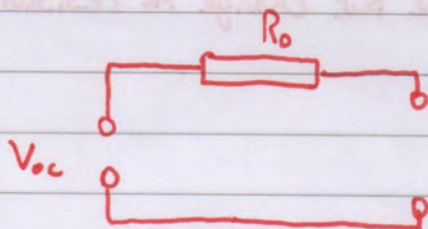


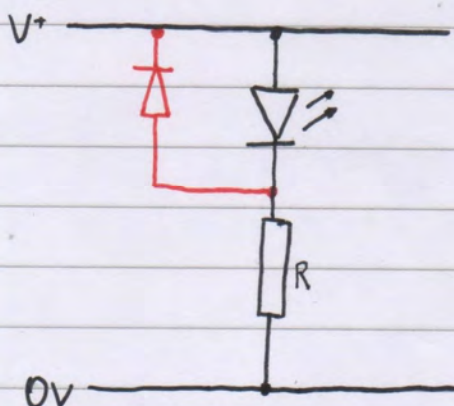You will usually need to draw the Thevenin equivalent



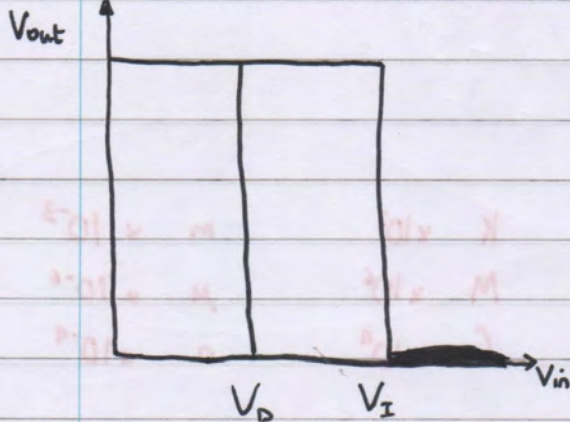
- This always assumes  $2V$  used across LED
- $R = \frac{V^+ - 2}{I}$
- Diode (in red) protects from reverse polarity of AC supply
- $\frac{1}{2} R$  is resistance for AC circuit






- $V_I$  is increasing input voltage threshold
- $V_D$  is decreasing input voltage threshold


### Schmitt inverter as astable

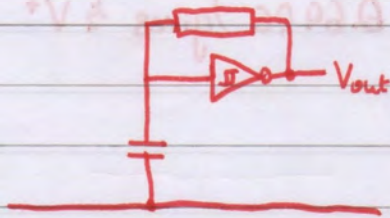

### Schmitt inverter as debouncer


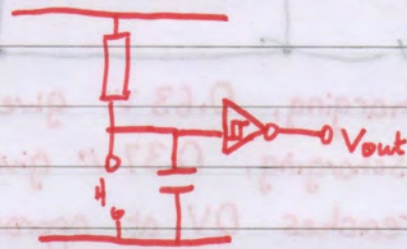


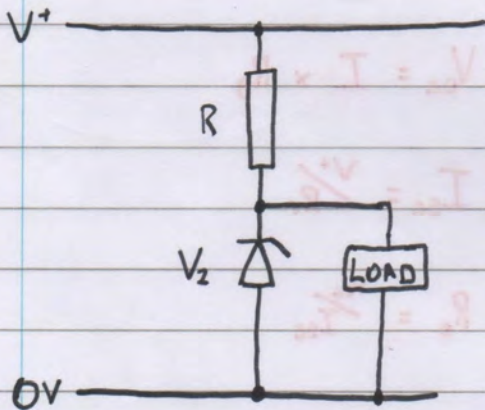- Schmitt inverters can be used as debouncers to stop flickering




- $V_R = V^+ - V_Z$
- Add all currents given for  $I$
- $R = \frac{V}{I}$

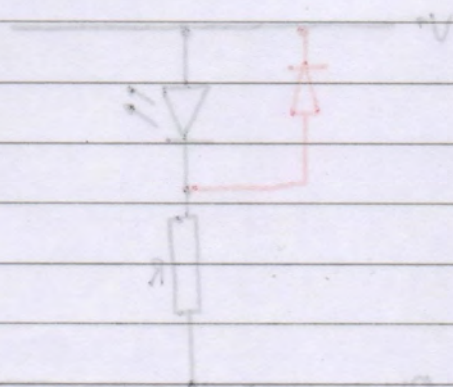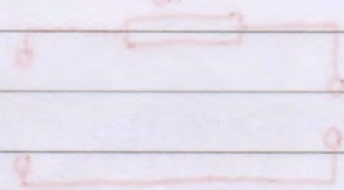- If  $V^+$  changes, keep the load voltage the same but change the resistor voltage






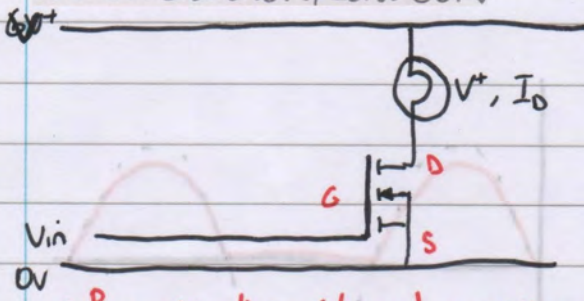


- $V_{GS}$  is input voltage
- $V_{GS}$  or  $G_m$  will be given to you
- $I_D = V_{GS} G_m$

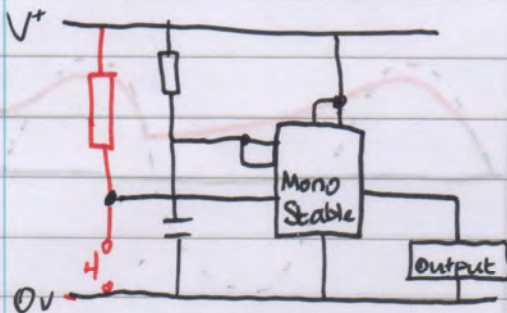- $R_{DS}$  is the internal resistance
- Power =  $I_D \times R_{DS}$
- MOSFETs need a low  $R_{DS}$  for lower power consumption
- Estimate gate current will be 0A




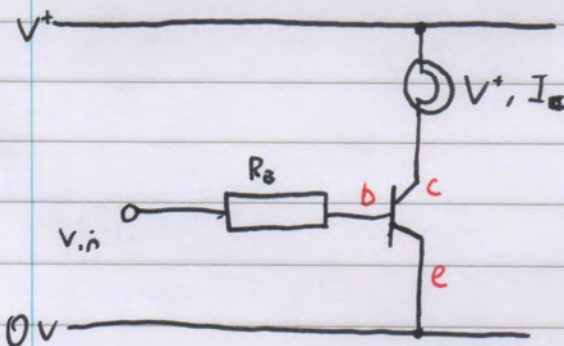- To make the SSS negative-edge triggered, add resistor on top and switch on bottom
- Resistor on top and capacitor on bottom for capacitance
- $T = 1.1 RC$




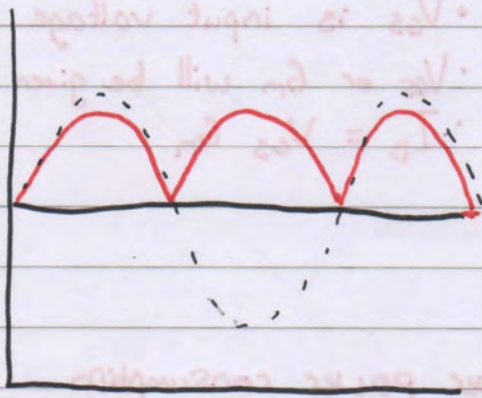- $I_c = I_b h_{FE}$
- $R_B = \frac{V_{in} - 0.7}{I_b}$
- Power =  $I_c \times V_{out}$







Unsmoothed Full-Wave

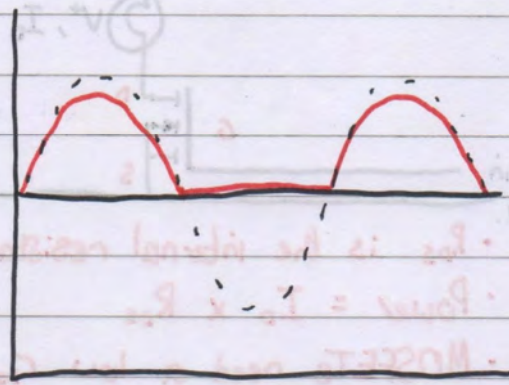

Unsmoothed Half-Wave

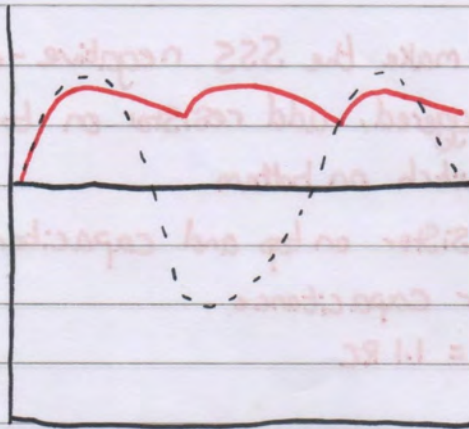

Smoothed Full-Wave

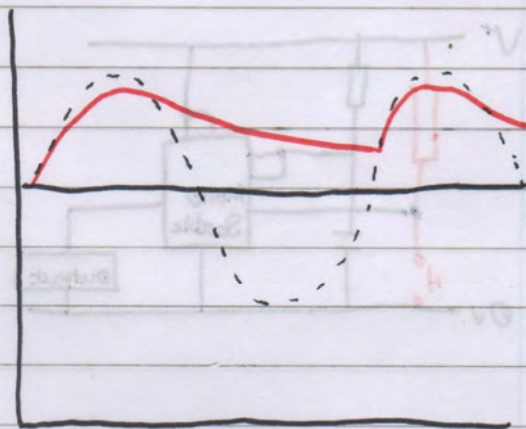

Smoothed Full-Wave

$$I_C = I_o$$

$$R_o = \frac{V_o - V_D}{I_o}$$

$$P_{out} = I_o \times V_o$$

